

Explanation of Precise Measurement of MS Series Resistors

§0 . Abstract

The MS series products are resistors with alloy foil as the conductor. According to the classification of resistance value, they belong to low-resistance resistors. For the measurement of this type of resistors, it is necessary to choose a suitable circuit to eliminate the impact of wire resistance, leakage current, temperature, etc. in the circuit in order to minimize errors and ensure measurement accuracy. The bridge method is a method of measuring with the comparative law, which is to compare the measured resistance with the standard resistance under balanced conditions to determine the accuracy of the to-be-tested resistor. With high sensitivity, accuracy, the bridge method is ingenious, convenient, and has low requirements for power supply stability. Thus it has been widely used in electrical technology and non-electrical measurement.

§1. Testing Principle

Wheatstone bridge: It is a bridge circuit proposed by Wheatstone in 1843. It consists of four resistors and a galvanometer. R_N is a precision resistor, and R_X is the resistor to be measured (Figure 1). After the circuit is connected, adjust R_1 , R_2 , R_N to make the current of the galvanometer zero, and the bridge is balanced. At this time, $R_X = R_1 \times R_N / R_2$. R_X is obtained by the exchange measurement method (exchange the position of R_N and R_X , and do not change R_1 , R_2).

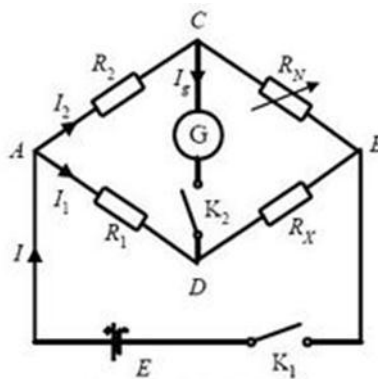


Fig.1: Wheatstone bridge circuit

Special contradiction in testing low resistance with Wheatstone bridge: The Wheatstone Bridge (single bridge) measures resistors, and its value is generally above 10 Ω. If a single bridge is used to measure low resistance, the additional resistances R' and R'' (lead resistor and terminal contact resistor, etc.) and R_X are directly connected in series (Figure 2), and the values of R' and R'' are equivalent to that of the measured resistor R_X and cannot be ignored. The resistance R_N is also a small resistor. Therefore, the formula $R_X = R_1 \times R_N / R_2$ for measuring resistance using a single bridge cannot accurately determine the value of R_X .

Explanation of Precise Measurement of MS Series Resistors

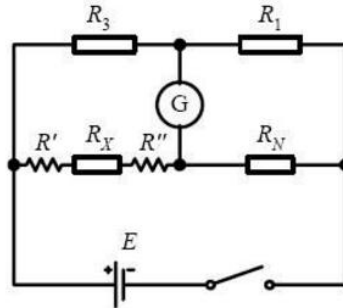


Fig.2: The effect of additional resistance on Wheatstone Single Bridge

Solution of Kelvin Double Bridge: Kelvin is the deformation of Wheatstone Bridge, which can give quite high accuracy when measuring small resistance. The structure is shown in Figure 3, where R_1 , R_2 , R_3 , and R_4 are all adjustable resistors, R_X is the measured low resistor, and R_N is the low value standard resistor. Compared with Wheatstone Single Bridge, Kelvin Bridge has made two important improvements:

- a. Added a bridge arm composed of R_2 and R_4 ;
- b. R_N and R_X changed from two end connection to four end connection ;

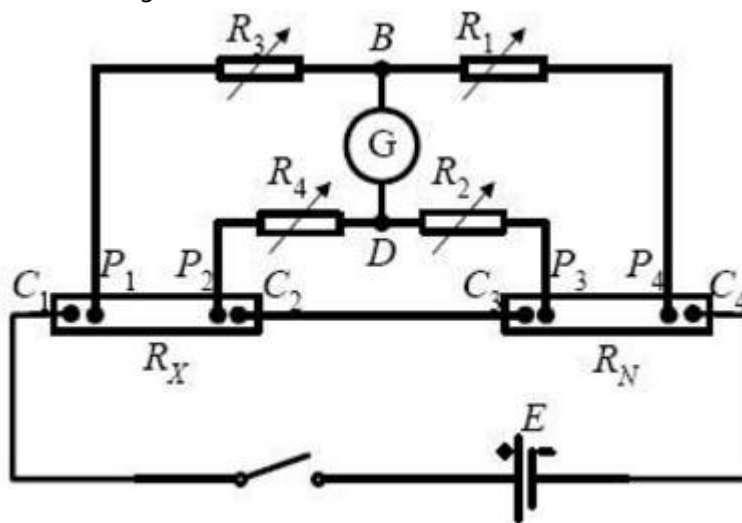


Fig.3: Schematic diagram of Kelvin Double Bridge

Among them, $P_1 P_2$ constitutes the measured low resistance R_X , $P_3 P_4$ is the standard low resistance R_N , $P_1 P_2$ and $P_3 P_4$ are often referred to as voltage contacts, $C_1 C_2$ and $C_3 C_4$ are called current contacts, cleverly transferring the wiring resistance and contact resistance of R_N and R_X to Internal resistance of the power supply and the bridge arm resistance with high resistance.

Explanation of Precise Measurement of MS Series Resistors


§2 . Test equipment



Test conditions :


Scale	Measurement range	Resolution	Measurement current	Accuracy	Open terminal voltage
1 mΩ	0.0000 mΩ ~ 1.5000 Ω	0.1 μΩ	3 A	Within ±(0.01% rdg + 1 μΩ) ± α digits	Appr. DC 4V
10 mΩ	0.000 mΩ ~ 15.000 Ω	1 μΩ	1 A		
100 mΩ	0.00 mΩ ~ 150.00 mΩ	10 μΩ			
1 Ω	0.0000 Ω ~ 1.5000 Ω	100 μΩ	100 mA		
10 Ω	0.000 Ω ~ 15.000 Ω	1 mΩ			
100 Ω	0.00 Ω ~ 150.00 Ω	10 mΩ	10 mA		
1 kΩ	0.0 Ω ~ 1500.0 Ω	100 mΩ	1 mA		

Wiring method :

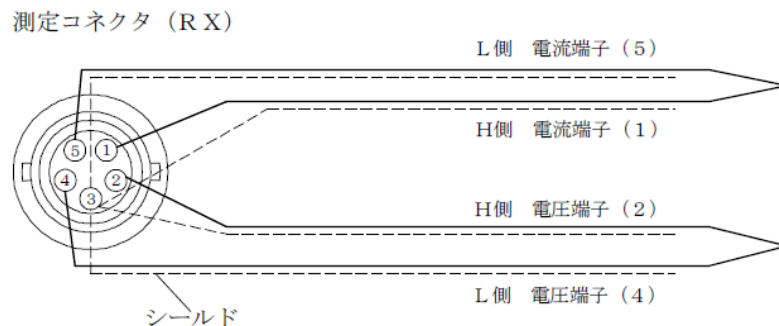

Explanation of Precise Measurement of MS Series Resistors

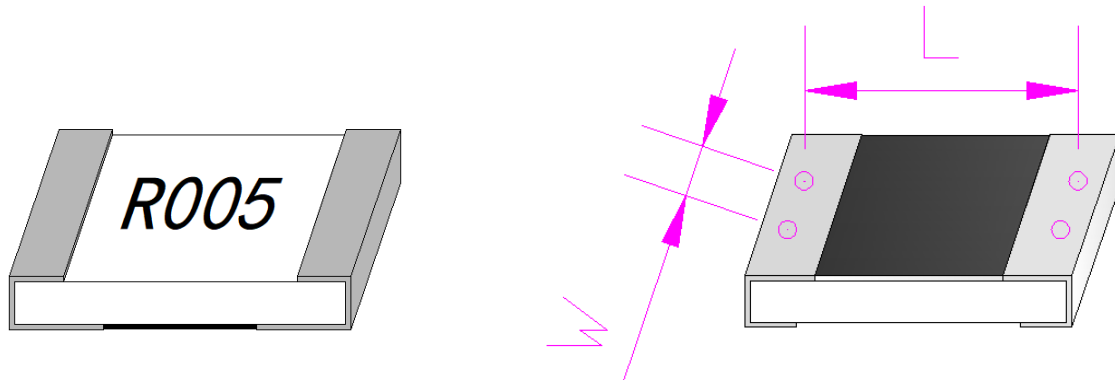§3 . Measuring position of MS series resistors



Measuring needle size :

No.	Spec.	Needle tip diameter (± 0.010)	Needle body diameter (± 0.010)	L (\pm 0.010)	W (\pm 0.010)
1	0402	0.080	0.200	0.700	0.120
2	0603	0.100	0.200	1.050	0.400
3	0805	0.100	0.300	1.650	0.35
4	1206	0.100	0.350	2.600	0.800
5	2512	0.100	0.350	5.300	1.000
6	2010	0.100	0.350	4.300	0.500

§4. Summary

When measuring the resistance value of MS series resistors, it is necessary to pay attention to the following points: ensure that the testing instrument is grounded to reduce interference, and try to maintain stability during the testing process to reduce errors caused by poor contact.